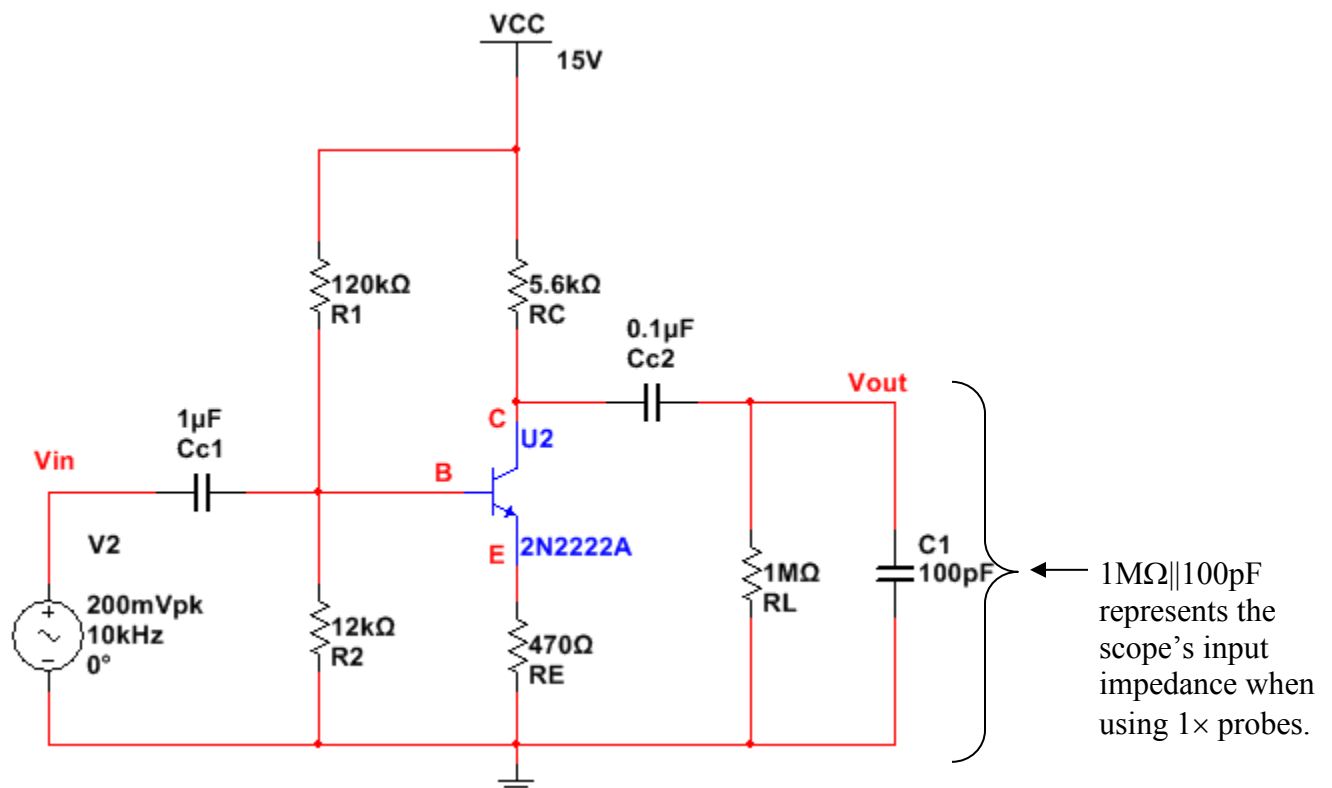


## CE Frequency Response

1. A CE amplifier circuit is shown below. The BJT has  $\beta = 220$ ,  $r_\pi = 4.2\text{k}\Omega$ ,  $r_o = 76\text{k}\Omega$ ,  $r_x = 0.13\Omega$ ,  $g_m = 52\text{mS}$ ,  $C_\pi = 27\text{pF}$  and  $C_\mu = 9\text{pF}$ . Estimate the mid-band voltage gain using Equation (7.111):

$$A_{vo} = -\frac{g_m R_C}{1 + g_m R_E}$$

Use the SCTC method to determine values for  $C_{C1}$  and  $C_{C2}$  that result in  $f_L \cong 20\text{Hz}$ . Assign 90% to the dominant  $\tau$ . Note:  $C_1 = 100\text{pF}$  presents a high reactance at low frequencies. It is the parasitic capacitance of the scope cable and, like the BJT parasitic capacitances, it is modeled as an open circuit at low to mid-band frequencies. Use the OCTC method to estimate the value for  $f_H$ .



### Lower 3-dB Frequency, $f_L$

2. Build the circuit. Set up a 400mV peak-to-peak, 10 kHz sin wave and use 1× probes to measure the circuit's mid-band voltage gain,  $A_{vo} = v_{out}/v_{in}$ . Compare with your pre-lab estimate.

3. Reduce the signal frequency until  $v_{out}$  falls to 70.7% of its mid-band value. How close is your measured value for  $f_L$  to the SCTC estimate?

### Upper 3-dB Frequency, $f_H$

4. Increase the signal frequency beyond 10 kHz until  $v_{out}$  again falls to 70.7% of its mid-band value. How close is your measured value for  $f_H$  to the OCTC estimate? Switch to 10× probes and re-measure  $f_H$ . Explain your results.